
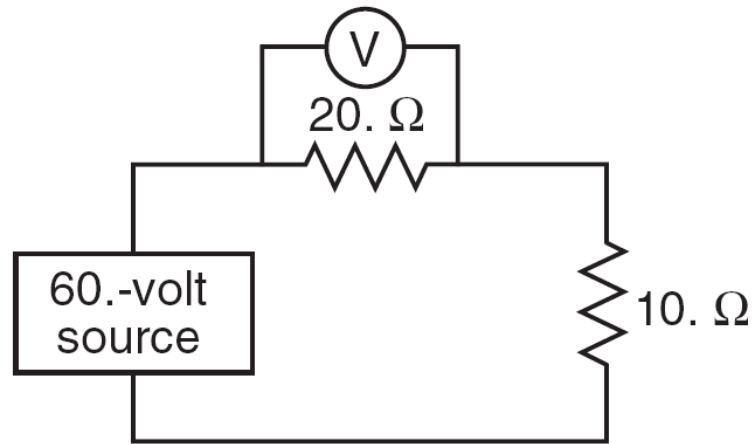


b) Current in this circuit?

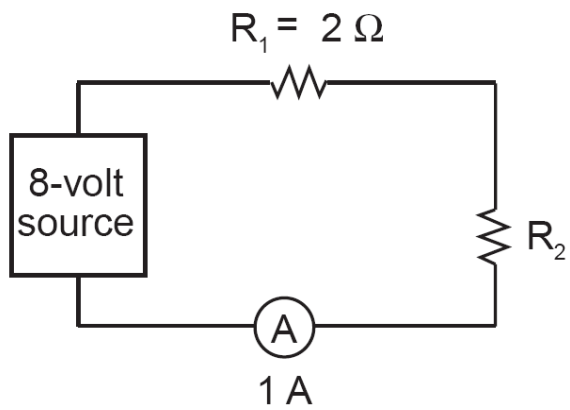


c) Potential difference in 20 ohm resistor?

Ex 10) Find R_2



a) $I_1 = ?$

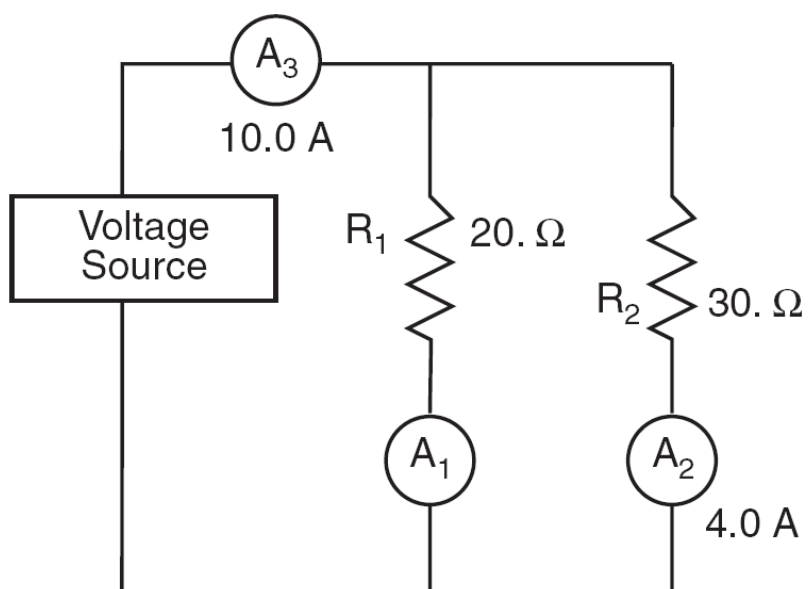

b) $V_T = ?$